 



CS 223 PROJECT
TARIK BUĞRA KARALI
ID: 21703937
SECTION :1



CS CamScanner ile tarandı

Datapath-controller

The picture given below is demonstrates that datapath- controller of single cycle processor. The controller determines the conditions by signals. Execution signal determines the instruction which will be used for operations takes value from swithces or instruction memory. Write enable is controls the data written or not on data memory and write reg enable controls the data written or not on register. Also the Alu control takes the instruction and signals from the controller and according the signals condition, instruction is divided properly to send data memory or register or both of them as inputs. Also the add signal controls the sum operation from the register's data at the sepecified addresses. Seven segment display shows the data memory on board. Instruction memory holds the instruction written by user.

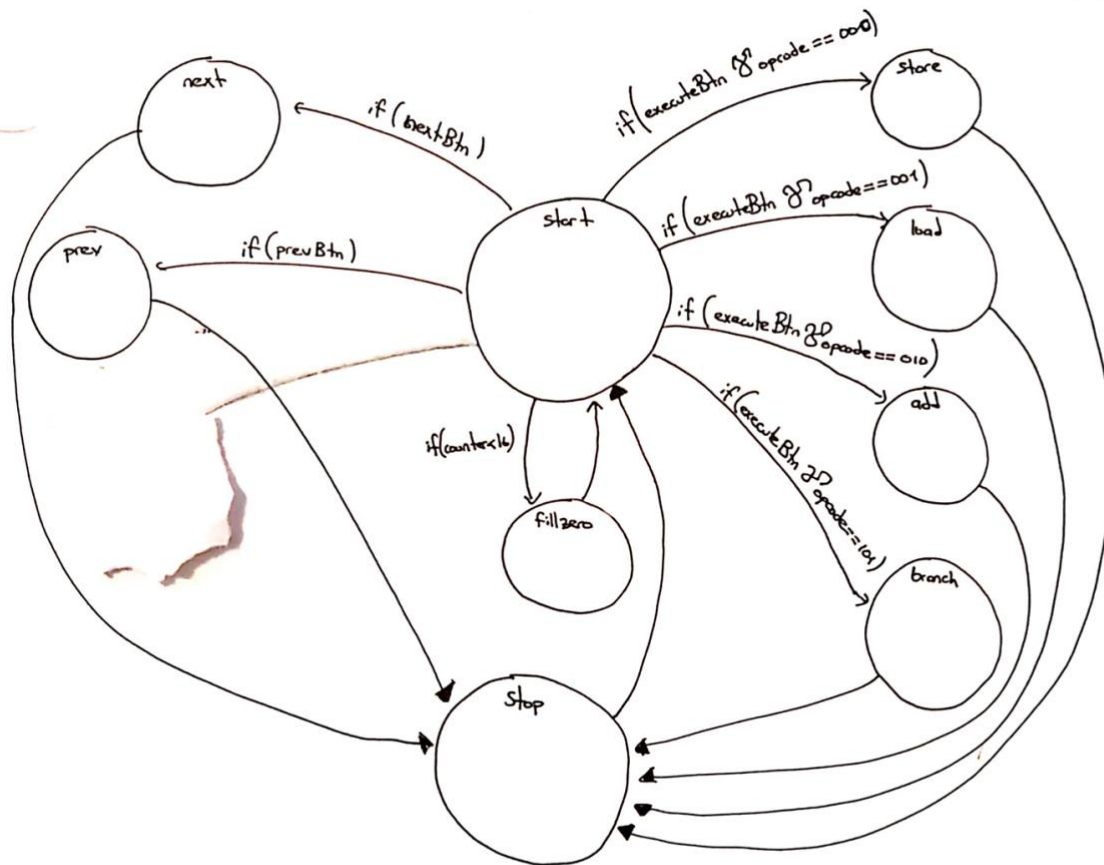

State Diagram

The state diagram given below demonstrates the top down designs work logic. Start condition goes to fillzero in order to ensure the data memory have 8'b00000000 elements on initial condition or after the reset. Then the pulse taken from the buttons determines the next state. If the execute command is delivered (middle button), value of the opp code is determines the next state and in the store, load, add, branch states apply the operation according to instruction. After the operation done, that states goes the stop and then goes to start state. It means that machine get ready to new command. Also if the next command is delivered (right button), the next state is increment the memory address; if the previous command is delivered (left button), the next state is decrement the memory address and the operations seen in the seven segment display. If the down button is pressed, instruction is taken from instruction memory in the start state and again after the determining opcode, appropriate operation will be executed. The upper button is represent the reset and if the reset is pushed, next state will be start and counter takes the zero value so the data memory, register and instruction memory turns the initial condition.

Debounce: This module detect the button pressed and turns them to a pulse.

```
module debounce( input logic clk,
                 input logic button,
                 output logic pulse );

    logic [24:0] timer;
    typedef enum logic [1:0]{S0,S1,S2,S3} states;
    states state, nextState;
    logic gotInput;

    always_ff@(posedge clk)
        begin
            state <= nextState;
            if(gotInput)
                timer <= 25000000;
            else
                timer <= timer - 1;
        end
    always_comb
        case(state)
            S0: if(button)
                begin //startTimer
                    nextState = S1;
                    gotInput = 1;
                end
            else begin nextState = S0; gotInput = 0; end
            S1: begin nextState = S2; gotInput = 0; end
            S2: begin nextState = S3; gotInput = 0; end
            S3: begin if(timer == 0) nextState = S0; else nextState = S3; gotInput = 0; end
            default: begin nextState = S0; gotInput = 0; end
        endcase

    assign pulse = ( state == S1 );
endmodule
```

Instruction Mememory: This module holds the instruction and capable of carry 32 instruction.

```
module InstructionMem( input logic [2:0]opcode,
                     input logic [12:0]remain,
                     input logic [4:0] writeaddress,
                     input logic [4:0] address,
                     input logic reset,
                     input logic clock,
                     output logic [15:0] instruction
);

    logic [15:0] IM [31:0];

    always_ff @ (posedge clock, posedge reset)
        begin
            if(reset)
```

```

    for( int j = 0; j <= 16; j++)
    begin
        IM[j] = 16'b0000_0_0000_0000_0001;
    end

    else
        IM[writeaddress] [15:13] = opcode;
        IM[writeaddress] [12:0] = remain;
        instruction <= IM[address] ;
    end
endmodule

Register:
module register( input logic clock,
input logic [3:0] writeAddress,
input logic [7:0] writeData,
input logic writeEnable,
input logic reset,
input logic [3:0] readAddress1, readAddress2,
output logic [7:0] readData1, readData2
);
logic [7:0] mem[15:0] ;

logic enable;
logic [7:0] data;
logic [3:0] address;
logic [3:0] readAdd1, readAdd2;
logic [7:0] readDat1, readDat2;

assign enable = writeEnable;
assign data = writeData;
assign address = writeAddress;
assign readAdd1 = readAddress1;
assign readAdd2 = readAddress2;

//always_comb
always_ff @ (posedge clock)
begin
    if(reset)
        for( int j = 0; j <= 16; j++)
            begin
                mem[j] = 8'b00000000;
            end
    if( writeEnable ) mem[writeAddress] <= writeData;

    readData1 <= mem[readAddress1];
    readData2 <= mem[readAddress2];
end
endmodule

Data Memory:
module memory( input logic clock,

```

```

input logic [3:0] writeAddress,
input logic [7:0] writeData,
input logic writeEnable,
input logic reset,
input logic [3:0] readAddress1, readAddress2,
output logic [7:0] readData1, readData2
);
logic [7:0] mem[15:0] ;

```

```

logic enable;
logic [7:0] data;
logic [3:0] address;
logic [3:0] readAdd1, readAdd2;
logic [7:0] readDat1, readDat2;

```

```

assign enable = writeEnable;
assign data = writeData;
assign address = writeAddress;
assign readAdd1 = readAddress1;
assign readAdd2 = readAddress2;

```

```

//always_comb
always_ff @ (posedge clock)
begin
    if(reset)
        for( int j = 0; j <= 16; j++)
            begin
                mem[j] = 8'b00000000;
            end
    if( writeEnable ) mem[writeAddress] <= writeData;

```

```

readData1 <= mem[readAddress1];
readData2 <= mem[readAddress2];
end
endmodule

```

Seven Segment Display:

```

module SevSeg_4digit(
    input clk,
    input [3:0] in3, in2, in1, in0, //user inputs for each digit (hexadecimal value)
    output [6:0]seg, logic dp, // just connect them to FPGA pins (individual LEDs).
    output [3:0] an // just connect them to FPGA pins (enable vector for 4 digits active low)
);

```

// divide system clock (100Mhz for Basys3) by 2^N using a counter, which allows us to multiplex at lower speed

```

localparam N = 18;
logic [N-1:0] count = {N{1'b0}}; //initial value
always@ (posedge clk)
    count <= count + 1;

```

```
logic [4:0]digit_val; // 7-bit register to hold the current data on output
logic [3:0]digit_en; //register for the 4 bit enable
```

```
always@ (*)
```

```
begin
```

```
    digit_en = 4'b1111; //default
```

```
    digit_val = in0; //default
```

```
    case(count[N-1:N-2]) //using only the 2 MSB's of the counter
```

```
        2'b00 : //select first 7Seg.
```

```
        begin
```

```
            digit_val = {1'b0, in0};
```

```
            digit_en = 4'b1110;
```

```
        end
```

```
        2'b01: //select second 7Seg.
```

```
        begin
```

```
            digit_val = {1'b0, in1};
```

```
            digit_en = 4'b1101;
```

```
        end
```

```
        2'b10: //select third 7Seg.
```

```
        begin
```

```
            digit_val = {1'b1, in2};
```

```
            digit_en = 4'b1011;
```

```
        end
```

```
        2'b11: //select forth 7Seg.
```

```
        begin
```

```
            digit_val = {1'b0, in3};
```

```
            digit_en = 4'b0111;
```

```
        end
```

```
    endcase
```

```
end
```

```
//Convert digit number to LED vector. LEDs are active low.
```

```
logic [6:0] sseg_LEDs;
```

```
always @(*)
```

```
begin
```

```
sseg_LEDs = 7'b1111111; //default
```

```
case( digit_val)
```

```
    5'd0 : sseg_LEDs = 7'b1000000; //to display 0
```

```
    5'd1 : sseg_LEDs = 7'b1111001; //to display 1
```

```
    5'd2 : sseg_LEDs = 7'b0100100; //to display 2
```

```
    5'd3 : sseg_LEDs = 7'b0110000; //to display 3
```

```
    5'd4 : sseg_LEDs = 7'b0011001; //to display 4
```

```
    5'd5 : sseg_LEDs = 7'b0010010; //to display 5
```

```
    5'd6 : sseg_LEDs = 7'b0000010; //to display 6
```

```
    5'd7 : sseg_LEDs = 7'b1111000; //to display 7
```

```

5'd8 : sseg_LEDs = 7'b00000000; //to display 8
5'd9 : sseg_LEDs = 7'b0010000; //to display 9
5'd10: sseg_LEDs = 7'b0001000; //to display a
5'd11: sseg_LEDs = 7'b0000011; //to display b
5'd12: sseg_LEDs = 7'b1000110; //to display c
5'd13: sseg_LEDs = 7'b0100001; //to display d
5'd14: sseg_LEDs = 7'b0000110; //to display e
5'd15: sseg_LEDs = 7'b0001110; //to display f
5'd16: sseg_LEDs = 7'b0110111; //to display "="
default : sseg_LEDs = 7'b0111111; //dash
endcase
end

```

```

assign an = digit_en;
assign seg = sseg_LEDs;
assign dp = 1'b1; //turn dp off

```

endmodule

ALU:

```

module ALU(  input logic clk,
             input logic [3:0] opcode,
             input logic [12:0] instruction,
             input logic pressed,
             output logic [7:0] write_reg_data,
             output logic [3:0] write_reg_address,
             output logic [3:0] read_reg_address,
             output logic [7:0] read_reg_data,
             output logic [7:0] write_data,
             output logic [3:0] write_address,
             output logic [3:0] read_address1,
             output logic [3:0] read_address2,
             output logic [7:0] read_data1,
             output logic [7:0] read_data2
);

```

```

always @(*)
begin
case(opcode)
3'b000: // Store0
begin
if(pressed)
begin
if(instruction[12] == 0 ) //Immediate bit
begin
read_reg_address = instruction [7:4];
write_data = read_reg_data;
write_address = instruction [3:0];
end

```

if(instruction[12] == 1) //Immediate bit


```

begin
    write_address = instruction [11:8];
    write_data = instruction [7:0];
end
end
end
3'b001: // data_processing
begin
    if(pressed)
    begin
        if(instruction[12] == 0 ) //Immediate bit
        begin
            read_address1 = instruction [7:4];
            write_reg_address = instruction [7:4];
            write_reg_data = read_data1;
        end

        if(instruction[12] == 1 ) //Immediate bit
        begin
            write_reg_data = instruction [7:0];
            write_reg_address = instruction [11:8];
        end
    end
end
default: begin
    read_reg_address = instruction [7:4];
    write_data = read_reg_data;
    write_address = instruction [3:0];
end
endcase
end

```

endmodule

Top Design:

```

module topDesign( input logic clk, reset,
    input logic [2:0] opcode,
    input logic [12:0] instruction,
    input logic nextDisplay, prevDisplay, executDisplay, show,
    output logic [15:0] led,
    output [6:0] seg, logic dp,
    output [3:0] an
    );

    logic nextBtn;
    logic prevBtn;
    logic executeBtn;
    logic resetBtn;
    logic showBtn;

    debounce buttonNextDebouncer( clk, nextDisplay, nextBtn);
    debounce buttonPreviousDebouncer( clk, prevDisplay, prevBtn);
    debounce buttonMiddleDebouncer( clk, executDisplay, executeBtn );

```

```
debounce buttonResetDebouncer( clk, reset, resetBtn );
debounce buttonDownDebouncer( clk, show, showBtn );
```

```
//IM variables
```

```
logic [4:0] current_IM_address;
logic [4:0] write_im_address;
logic [4:0] readIMAddress;
logic [15:0] readDataIM;
```

```
//DataMem variables
```

```
logic [3:0] write_address;
logic [7:0] write_data;
logic [7:0] readData1;
logic [7:0] readData2;
logic writeEnable;
logic [3:0] read_address1;
logic [3:0] read_address2;
```

```
//Reg variables
```

```
logic writeRegEnable;
logic [3:0] read_reg_address1;
logic [3:0] read_reg_address2;
logic [3:0] write_reg_address;
logic [7:0] read_reg_data1;
logic [7:0] read_reg_data2;
logic [7:0] write_reg_data;
```

```
//control
```

```
logic executeSignal;
```

```
assign led = readDataIM;
```

```
InstructionMem im( opcode,instruction, write_im_address,current_IM_address, reset,clk,
readDataIM);
```

```
memory dataMem( clk,write_address, write_data, writeEnable, reset, read_address1,
read_address2, readData1, readData2 );
```

```
register rf( clk,write_reg_address, write_reg_data, writeRegEnable , reset, read_reg_address1,
read_reg_address2, read_reg_data1,read_reg_data2 );
```

```
SevSeg_4digit sev( clk, read_address1, 0, readData1[7:4], readData1[3:0], seg, dp, an);
```

```
typedef enum logic [3:0] { start,fillzero, store, load, add, branch, stop, next, prev } statetype;
statetype [3:0] state, nextstate;
```

```
logic [4:0] counter = 0;
```

```
always_ff @ ( posedge clk)
```

```
begin
```

```
if( resetBtn )
```

```
begin
```

```
state <= start;
```

```
current_IM_address <= 0;
```

```
end
```

```

else
    state <= nextstate;

case( state)
start:
begin
    writeEnable = 0;
    writeRegEnable = 0;
    write_im_address = 0;
    readIMAddress = current_IM_address;
    if (counter < 16) nextstate = fillzero;
    else
    begin
        if( executeBtn )
        begin
            executeSignal = 1;
            write_im_address =(write_im_address + 5'd1);

            if( opcode == 3'b000 )nextstate = store;
            else if( opcode == 3'b001 )nextstate = load;
            else if( opcode == 3'b010)nextstate = add;
            else if( opcode == 3'b101)nextstate = branch;
            else if( opcode == 3'b111 )nextstate = stop;
        end

        else if( nextBtn ) nextstate = next;
        else if( prevBtn ) nextstate = prev;
        else if( showBtn )
        begin
            if( readDataIM[15:13] == 3'b000)nextstate = store;
            else if( readDataIM[15:13] == 3'b001) nextstate = load;
            else if( readDataIM[15:13] == 3'b010)nextstate = add;
            else if( readDataIM[15:13] == 3'b101)nextstate = branch;
        end

        else
        begin
            nextstate = start;
        end
    end
end
end

fillzero:
begin
    writeEnable = 1;
    write_address <= counter;
    writeRegEnable = 1;
    write_reg_address <= counter;
    write_reg_data <= 0;
    counter = counter + 1;
    nextstate = start;
end

```

```

end

store:
begin
    writeEnable = 1;
    if( executeSignal == 1)
    begin
        if( instruction[12] == 1 )
        begin
            write_address = instruction [11:8];
            write_data = instruction[7:0];

            read_address1 = write_address;
        end

        else if ( instruction[12] == 0 )
        begin

            read_reg_address1 = instruction[3:0];
            write_address = instruction[7:4];
            write_data = read_reg_data1;
        end
    end
end

else if( executeSignal == 0 )
begin
    readIMAddress = current_IM_address;

    if( readDataIM[12] == 1 )
    begin
        write_address = readDataIM[11:8];
        write_data = readDataIM[7:0];
    end

    else if( readDataIM[12] == 0)
    begin
        read_reg_address1 = readDataIM[3:0];
        write_address = readDataIM[7:4];
        write_data = read_reg_data1;
    end

    if( current_IM_address == 32 )
        current_IM_address = 0;
    else
        current_IM_address = current_IM_address + 1;
    end

    executeSignal = 0;
    nextstate = stop;
end

```

```

load:
begin
    writeEnable = 0;
    writeRegEnable = 1;

    if ( executeSignal == 1 )
    begin
        if( instruction[12] == 1 )
        begin
            write_reg_address = instruction[11:8];
            write_reg_data = instruction[7:0];
        end

        else if ( instruction[12] == 0 )
        begin
            read_address2 = instruction[3:0];
            write_reg_address = instruction[7:4];
            write_reg_data = readData2;
        end

    end
    else if( executeSignal == 0 )
    begin
        readIMAddress = current_IM_address;

        if( readIMAddress[12] == 1 )
        begin
            write_reg_address = readDataIM[11:8];
            write_reg_data = readDataIM[7:0];
        end

        else if( readIMAddress[12] == 0 )
        begin
            read_address2 = readDataIM[3:0];
            write_reg_address = readDataIM[7:4];
            write_reg_data = readData2;
        end

        if( current_IM_address == 9 )
            current_IM_address = 0;
        else
            current_IM_address = current_IM_address + 1;

    end

    executeSignal = 0;
    nextstate = stop;
end

add:
begin
    writeRegEnable = 1;

```

```

if( executeSignal == 1 )
begin
    write_reg_address = instruction[11:8];
    read_reg_address1 = instruction[7:4];
    read_reg_address2 = instruction[3:0];
    write_reg_data = read_reg_data1 + read_reg_data2;
end

else if ( executeSignal == 0 )
begin
    readIMAddress = current_IM_address;
    write_reg_address = readDataIM[11:8];
    read_reg_address1 = readDataIM[7:4];
    read_reg_address2 = readDataIM[3:0];
    write_reg_data = read_reg_data1 + read_reg_data2;

    if( current_IM_address == 9 )
        current_IM_address = 0;
    else
        current_IM_address = current_IM_address + 1;

end

executeSignal = 0;
nextstate = stop;

end

branch:
begin
    if( executeSignal == 1 )
    begin
        read_reg_address1 = instruction[7:4];
        read_reg_address2 = instruction[3:0];

        if( read_reg_data1 == read_reg_data2 )
            current_IM_address = instruction[12:8];
        else
            begin
                if( current_IM_address == 32 )
                    current_IM_address = 0;
                else
                    current_IM_address = current_IM_address + 1;
                end
            end
        end

end

end

else if (executeSignal == 0 )
begin
    readIMAddress = current_IM_address;

```

```

    read_reg_address1 = readDataIM[7:4];
    read_reg_address2 = readDataIM[3:0];

    if( read_reg_data1 == read_reg_data2)
        current_IM_address = readDataIM[12:8];
    else
        begin
            if( current_IM_address == 9 )
                current_IM_address = 0;
            else
                current_IM_address = current_IM_address + 1;
            end
        end
    end

    executeSignal = 0;
    nextstate = stop;
end

stop:
begin
    nextstate = start;
end

next:
begin
    if( read_address1 == 'd15 )
        begin
            read_address1 = 0;
        end

    else
        begin
            read_address1 = read_address1 + (1'b1);
        end

        nextstate = stop;
    end

prev:
begin
    if( read_address1 == 0 )
        begin
            read_address1 = 'd15;
        end

    else
        begin
            read_address1 = read_address1 - (1'b1);
        end

        nextstate = stop;
    end
end

```

```
        default:
            nextstate = state;
        endcase
    end
endmodule
```